

# ***Clocks and Clock Generation***


John Morris  
Chung-Ang University  
The University of Auckland



**Iolanthe' at 13 knots on Cockburn Sound, Western Australia'**
 
# Clocks

- ❑ Clocks are a fundamental part of synchronous circuits
- ❑ With a large, complex circuit, management of the clock becomes a significant problem
  - ❑ Clock signals must
    - have fixed, known frequencies
      - Crystal oscillators are very stable
        - $f$  is temperature dependent
        - This only affects high precision ( $>1$  in  $10^5$ ) timing circuits
        - Crystal 'ovens' control  $T \Rightarrow$  very stable clocks
    - be 'clean'
      - ie* have sharp, well-defined edges
    - have low skew
      - Clock edge must arrive at all parts of the circuit simultaneously




# Clock Skew

- ❑ Correct operation of synchronous circuits assumes all circuits receive a clock edge at the same time


*ie* clock skew = 0

 - ❑ Physical characteristics of a real circuit make this impossible!
- ❑ Tolerance for clock skew
- ❑ Adds to the propagation delays
  - Signal generated by circuit reached last by a clock edge may be 'read' by a circuit which the clock reaches first
- ❑ Lengthens minimum cycle times
- ❑ Reduces potential operating frequency


 
# Clock Distribution

- ❑ Clock skew can be reduced by layout
  - ❑ Clock distribution trees
  - ❑ 'H' configurations
- ❑ Circuits derive clocks from the 'leaves' (endpoints) of the tree
  - ❑ Ideally, clock edges travel the same distance to each leaf
  - ❑ *and*
  - ❑ Arrive at the same time



 
# Clock Skew


- ❑ Amplifiers are commonly added
  - ⇒ Signal re-shaping
  - ⇒ 'Clean' clocks at all receivers
    - ⇒ 'Clean' = fast rise time!



- ❑ Although the clock may arrive at all 'receivers' at the same time
  - ⇒ At best, this will only occur on this device
- ❑ Clock skew (relative to other devices in a system) will now be high!




# Clock Skew

 

# Synchronizing clocks

 
## ❑ Phase locked loops (PLLs)

❑ Circuit blocks that 'lock' the phases of signals to a reference




❑ PLL adjusts phase of output so that the feedback signal and the reference are in phase

 
- Feedback could be derived from a 'leaf' of the clock tree
  - Output will be 'advanced' so that clocks at all leaves are in phase with the reference (and the rest of a system!)



# PLL structure

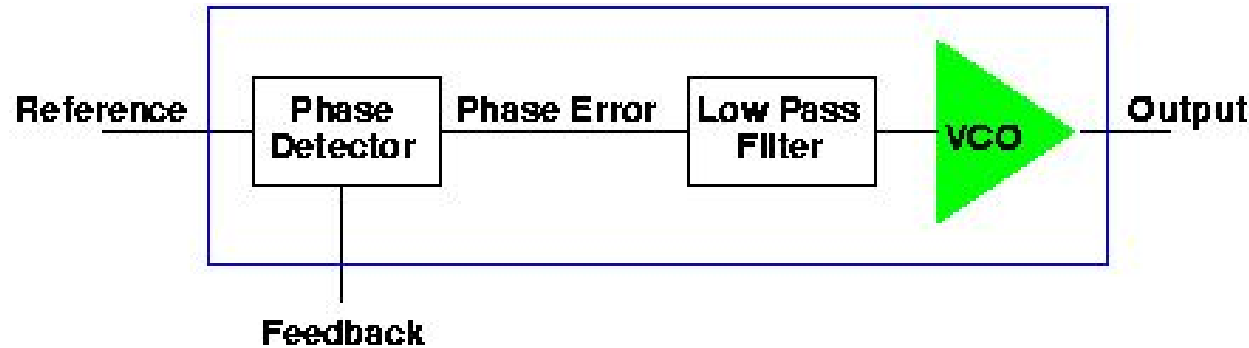

- ☐ Phase of Reference and feedback are compared
- ☐ Phase difference (error) drives a **Voltage Controlled Oscillator**
  - ☐ A VCO outputs a frequency proportional to its input voltage
  - ☐ Low Pass Filter restricts rate of change of VCO input
    - **Stops oscillatory behaviour**
- ☐ VCO outputs desired frequency
- ☐ Delays in the feedback cause
  - ☐ **Non zero phase error output, so the VCO frequency increases to 'catch up'**
- ☐ Eventually VCO will settle so that its frequency matches the reference and its phase ensures that the feedback and reference are 'phase locked'

 



# Frequency Multipliers

- ❑ Let's add a divider to the feedback

- ❑ Now, when the PLL has settled

- ❑  $f_{FB} / n = f_{ref}$   
and

- ❑  $\phi(FB) = \phi(ref)$


- ❑  $f_{output} = n \times f_{ref}$

or


- ❑ we have a **multiple** of the  $f_{ref}$  to drive our system

and

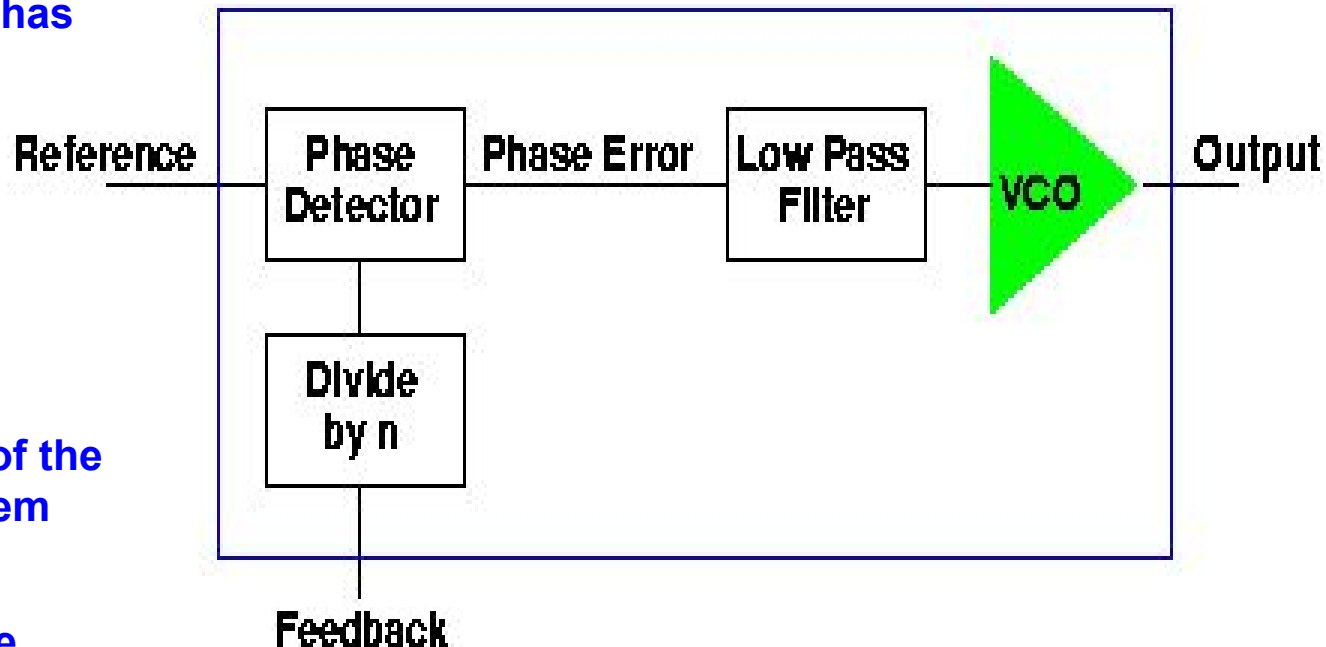- ❑ it's in phase with the reference
  - ❑ and the remainder of the system!




# Fractional PLLs

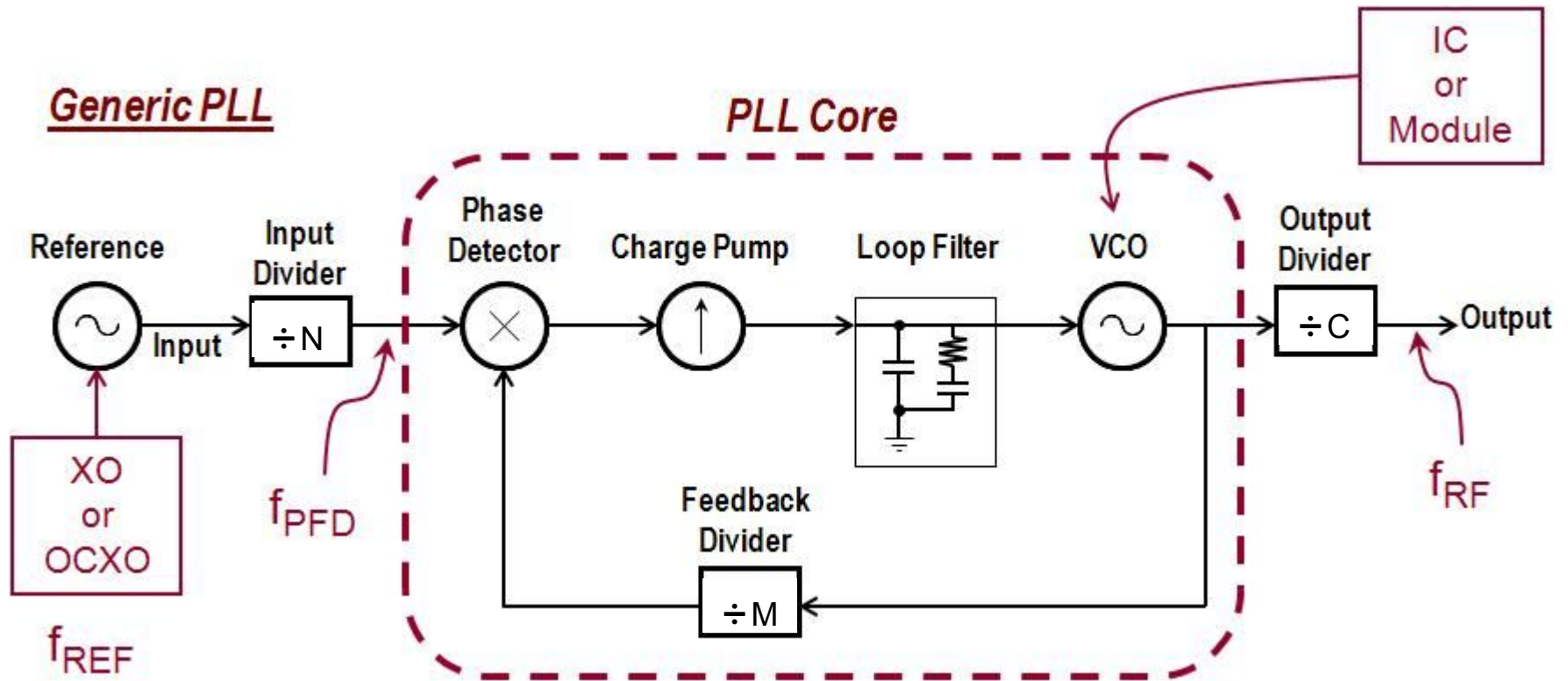


$$F_{RF} = F_{REF} * M / (N * C)$$

# Altera PLL Block Diagram

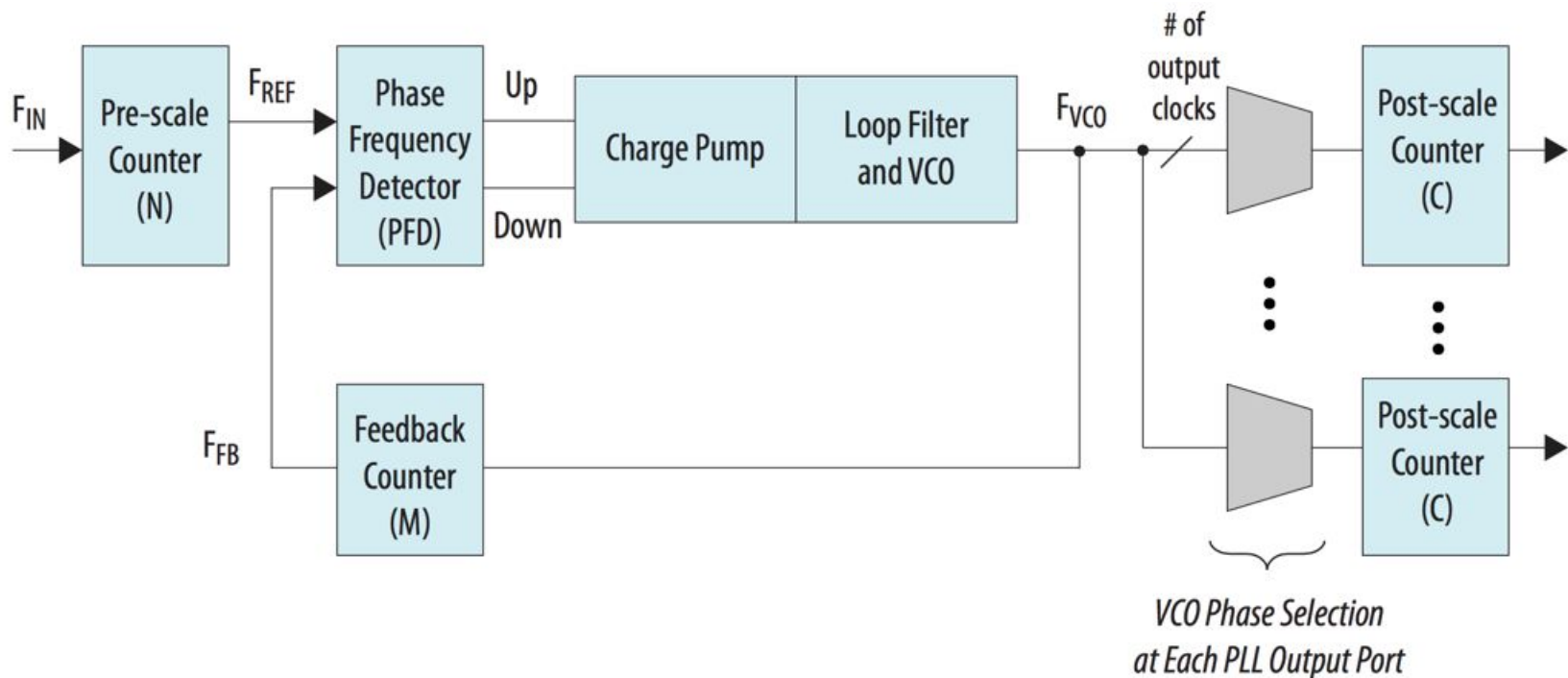

 
# Phase detectors

- An XOR gates produces a simple phase detector



- However, this doesn't indicate a 'lead' or a 'lag'
- A slightly more complex circuit produces 'up' and 'down' correction signals which can drive the VCO

# Altera PLL Module

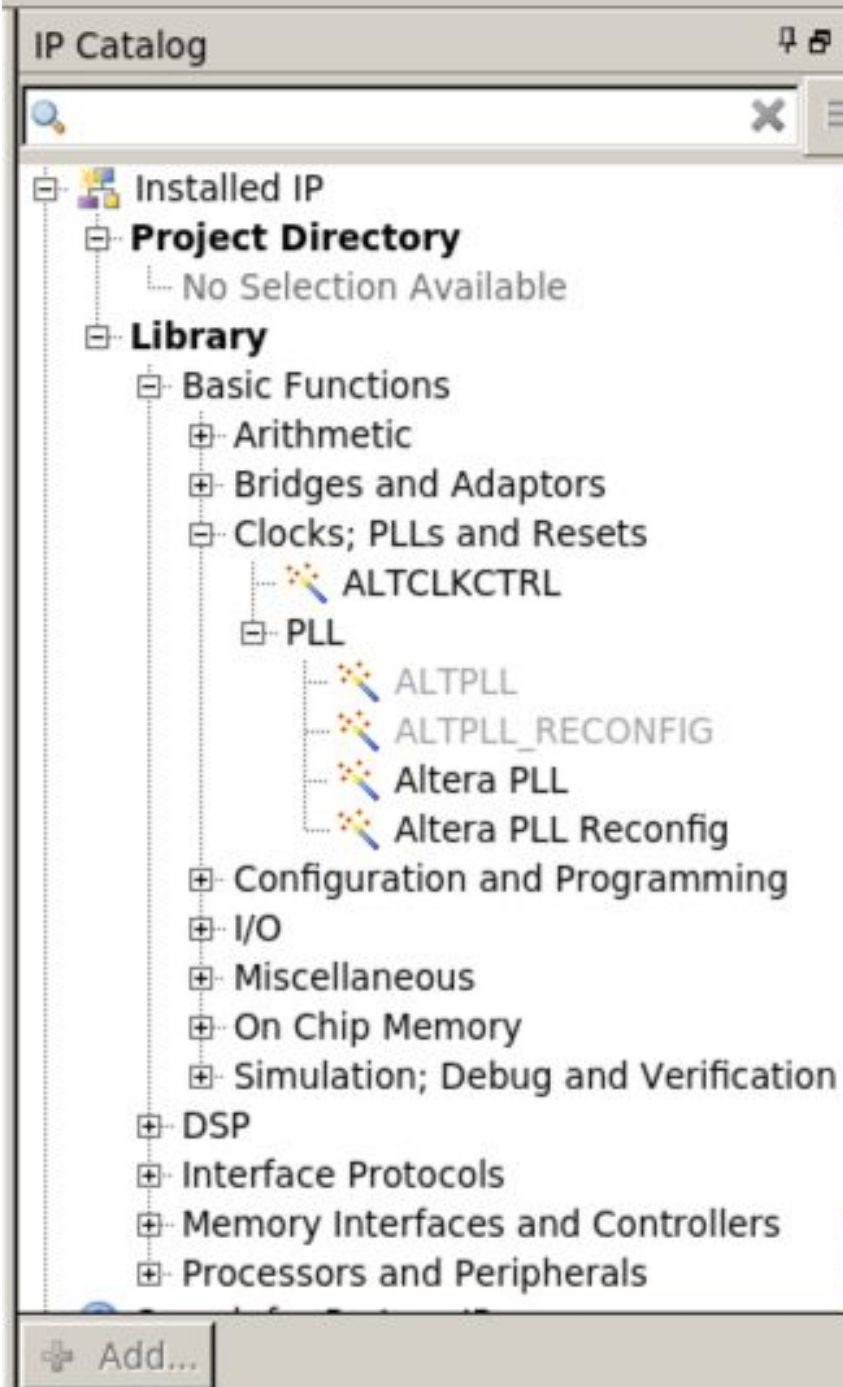




# Altera PLL

altera\_pll

[Documentation](#)

## Block Diagram

☐ Show signals

 

## General

Device Speed Grade:

6

PLL Mode:

Integer-N PLL

Reference Clock Frequency:

50.0 MHz

Operation Mode:

direct

☐ Enable locked output port

☐ Enable physical output clock parameters

## Output Clocks

Number Of Clocks:

1

### outclk0

Desired Frequency:

100.0 MHz

Actual Frequency:

100.000000 MHz

Phase Shift units:

ps

Phase Shift:

0 ps

Actual Phase Shift:

0 ps

Duty Cycle:

50 %

Copy


Info: **delete:** The legal reference clock frequency is 5.0 MHz..700.0 MHz

Cancel

Finish

# Altera PLL Modes

Parameter Names	Paramete...
M-Counter Hi Divide	3
M-Counter Low Divide	3
N-Counter Hi Divide	256
N-Counter Low Divide	256
M-Counter Bypass Enable	false
N-Counter Bypass Enable	true
M-Counter Odd Divide Enable	false
N-Counter Odd Divide Enable	false
C-Counter-0 Hi Divide	6
C-Counter-0 Low Divide	6
C-Counter-0 Coarse Phase Shift	1
C-Counter-0 VCO Phase Tap	0
C-Counter-0 Input Source	ph_mux_clk
C-Counter-0 Bypass Enable	false
C-Counter-0 Odd Divide Enable	false
VCO Post Divide Counter Enable	2
Charge Pump current (uA)	30
Loop Filter Bandwidth Resistor (O...	2000
PLL Output VCO Frequency	300.0 MHz
K-Fractional Division Value (DSM)	1
Feedback Clock Type	none
Feedback Clock MUX 1	glb
Feedback Clock MUX 2	m_cnt

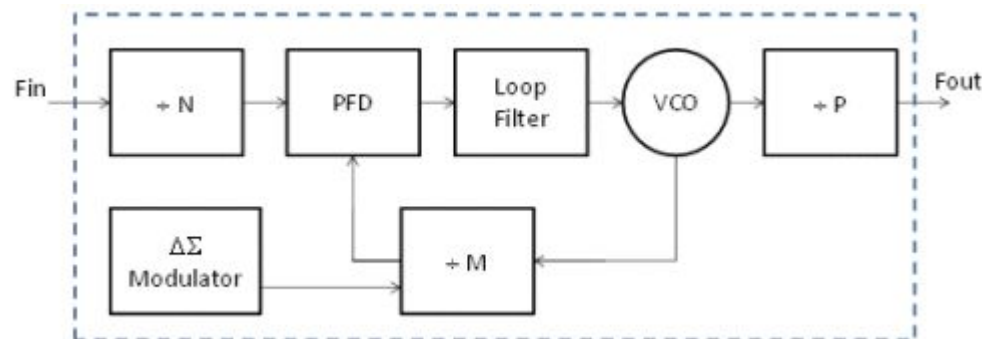

# ***PLL Uses***

- ❑ Thus PLLs
  - ❑ Keep clock edges aligned
  - ❑ Provide **multiples** of reference clocks
- ❑ You can drive your system with a low frequency clock
  - ❑ One you can drive over PCB tracks!
- ❑ FPGA internal clock frequencies can be much higher
  - ❑ Shorter distances, lower C allow higher  $f$ !
- ❑ Thus a PLL is a vital component of a high performance FPGA
  - ❑ Once it can support 'core' frequencies > ~300MHz




# PLL Uses

- ❑ Note that delays through the I/O buffers driving each pin are also significantly longer than, say, through a logic cell
  - ❑ For example, for an Altera FLEX10K10-3
    - Through a logic cell,  
 $\text{delay} = t_{\text{LUT}} + t_{\text{SU}} = 1.4 + 1.3 \text{ ns} = 2.7 \text{ ns}$
    - Through an I/O buffer,  
 $\text{delay} = t_{\text{IOD}} + t_{\text{OD1,2,3}} = 1.3 + (2.6 \text{ or } 4.9 \text{ or } 6.3) \text{ ns} = 3.9 - 7.6 \text{ ns}$
- ❑ This makes it hard to use an external clock  $> \sim 80\text{MHz}$  whereas internal circuits can be clocked up to nearly  $200\text{MHz}$
- ❑ PLLs to provide internal fast clocks are essential

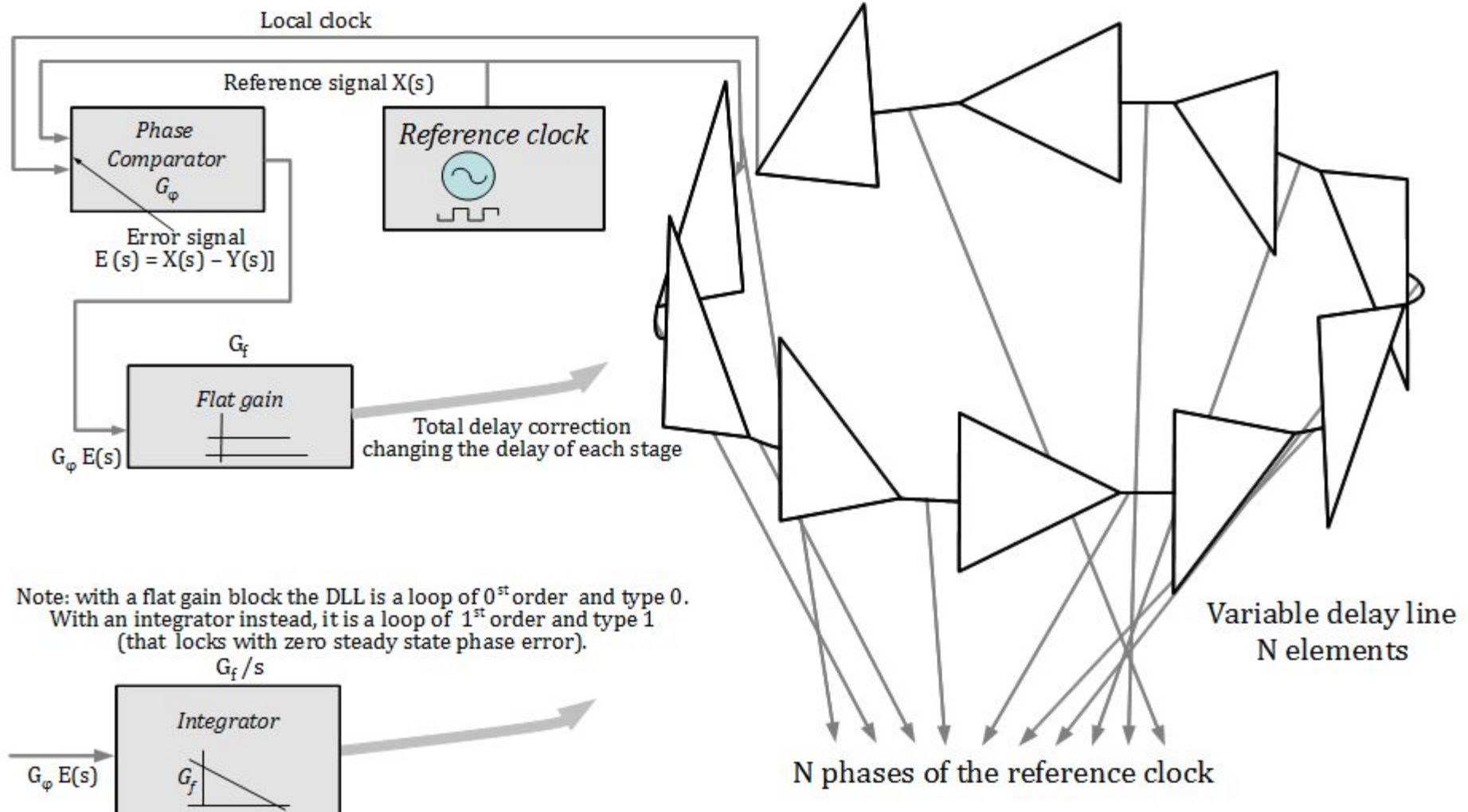
# Delay Locked Loop ( DLL )

A delay line whose total delay is locked to the clock period


 
# 'Rough' clocks

- We all know how to make an oscillator with an odd number of inverters



- Some FPGAs provide internal oscillators
  - ⇒ Clock without any external crystal
  - ⇒ However, the frequency of such clocks may vary widely
$$f \propto t_d(inv)$$
  - ⇒ Looking at the Altera data sheets
  - ⇒ For an EPF10K10-3,  $t_{LUT} \leq 1.4\text{ns}$
  - ⇒ For an EPF10K10-4,  $t_{LUT} \leq 1.7\text{ns}$

'Denotes the 'speed grade

# ***'Rough' clocks***

- ❑ **Speed grade?**
  - ❑ **Devices made on the same fabrication line**
  - ❑ **Tested**
  - ❑ **Binned (classified) as -3 or -4 depending on their performance, eg**
    - **If  $t_{\text{LUT}} \leq 1.4 \text{ ns}$ , it's a -3**
    - **If  $t_{\text{LUT}} > 1.4\text{ns}$ , it's a -4**
    - **If  $t_{\text{LUT}} > 1.7\text{ns}$ , it's a reject - or maybe a -5**
  - ❑ **This means that a “-4” device could have**  
 $1.4 \text{ ns} < t_{\text{LUT}} < 1.7\text{ns}$
  - ❑ **Thus an oscillator constructed in this way will have a frequency uncertainty of ~18%**  
*(based on as assumption of 1.7ns)*
- ❑ **So these internal oscillators are fine ..**

# ***'Rough' clocks***

❑ So these internal oscillators are fine

❑ If your design is

▪ (A)

- working with a **slow** asynchronous device
  - It must be slow enough so that you can clock a state machine much faster than the fastest response from the device and still guarantee any response times required by the device
- and
- has no critical output timing  
(*ie* you don't need to use the clock to accurately time an output)

▪ *or*

▪ (B)

- it's fast, but
- timing isn't critical  
(*ie* you can 'miss' an event in one clock cycle and detect it in the next without violating protocol rules)